

Implimentation of a full adder using multiplexer

For this implementation we are using two 4:1 multiplexers.

Truth table:

Input(A,B,C)

Output(Sum,Carry)

| A | B | C | Sum | Carry |
|---|---|---|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |


K-map for sum and carry:

Sum-

| C/AB | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |

Carry-

| C/AB | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |

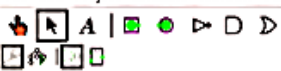

Circuit: main

| | |
|---------------------|--------------------|
| Circuit Name | main |
| Shared Label | |
| Shared Label Facing | East |
| Shared Label Font | SansSerif Plain 12 |

Implimentation of full adder using 4:1 multiplexer

